





AMERICAN RIVER COLLEGE

3 Phase Review





Transformers and 3-phase power

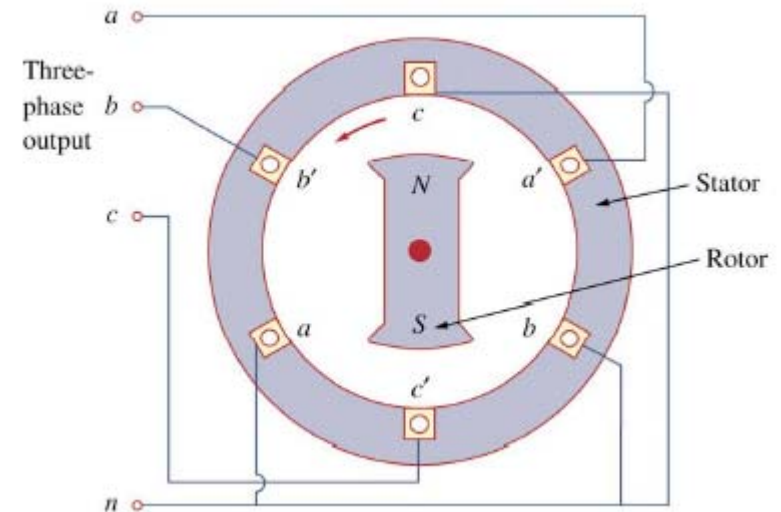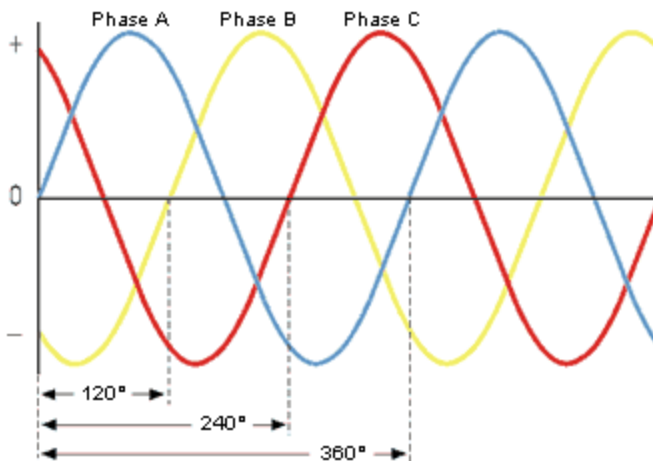- Why do we care?
- Where do we start?
 - AC/DC wars Who won, who lost, why?
 - How do generators and motors work?
 - How is electricity distributed today?



Transformers and 3-phase power

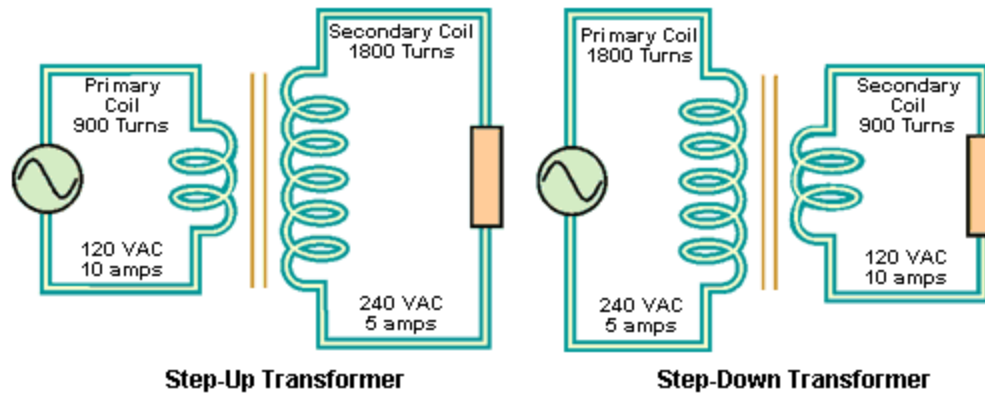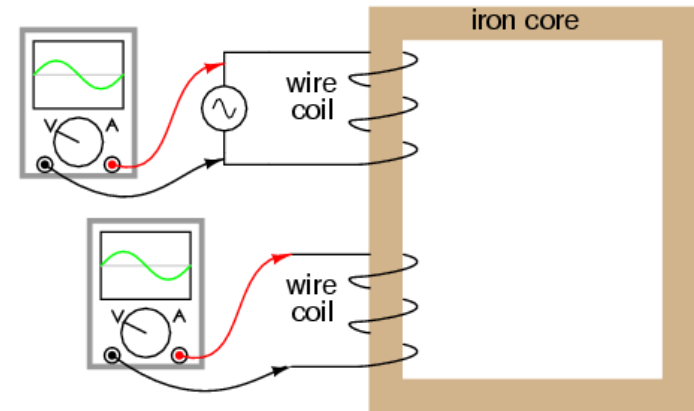
- What do transformers do?
- How do they work?
- Windings and Voltage
 - $V_1/N_1 = V_2/N_2$
 - $V_1/V_2 = N_1/N_2$





Transformers and 3-phase power

Energy Instructor

www.energyinstructor.info


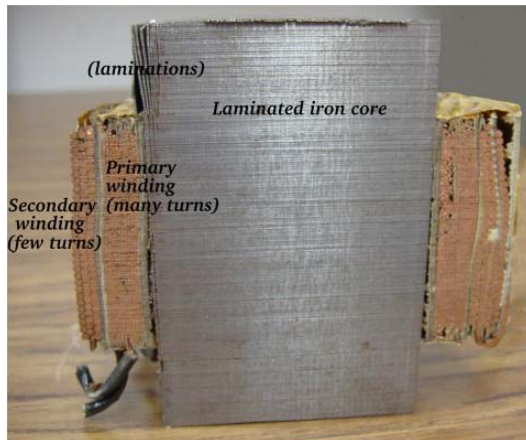


Transformers and 3-phase power

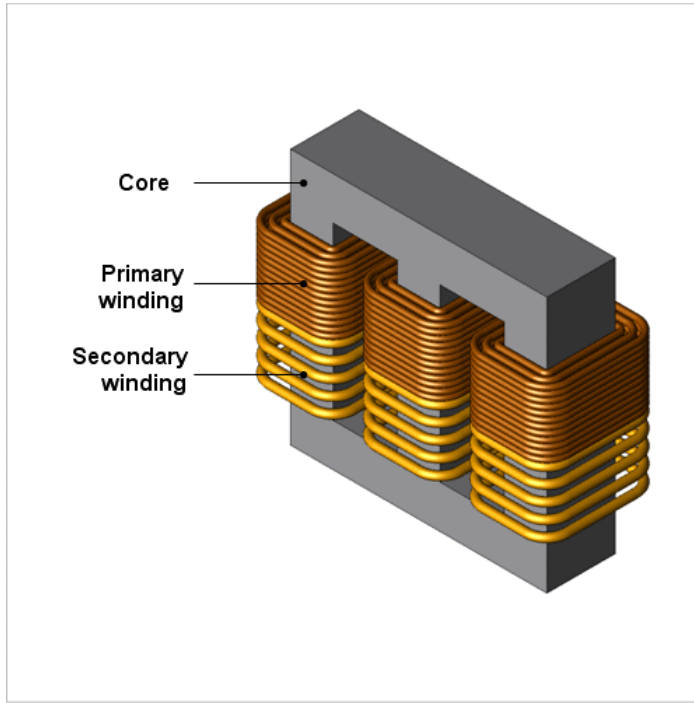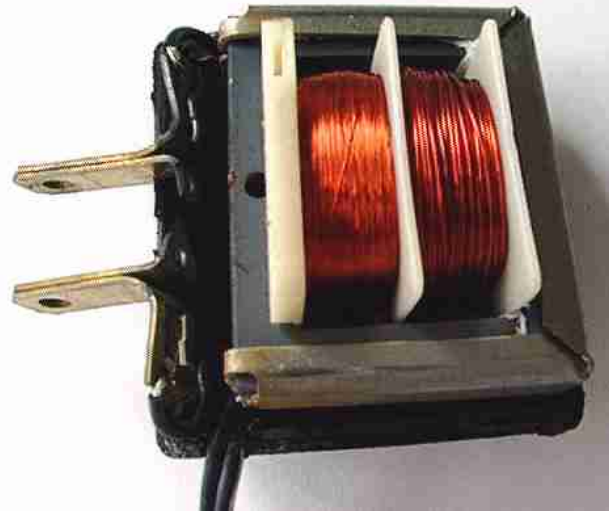



Transformers and 3-phase power

- Typical residential application

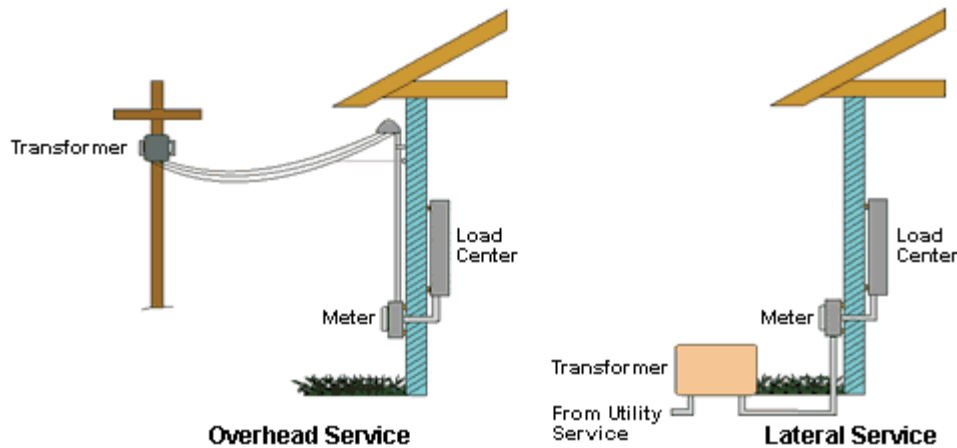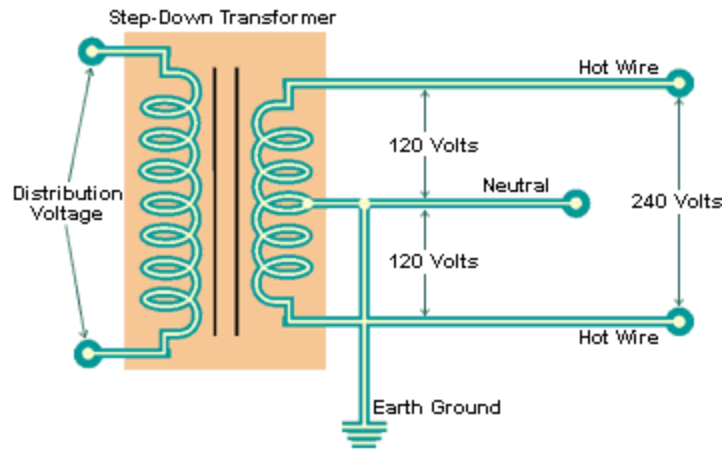


Transformers and 3-phase power

- Typical commercial application

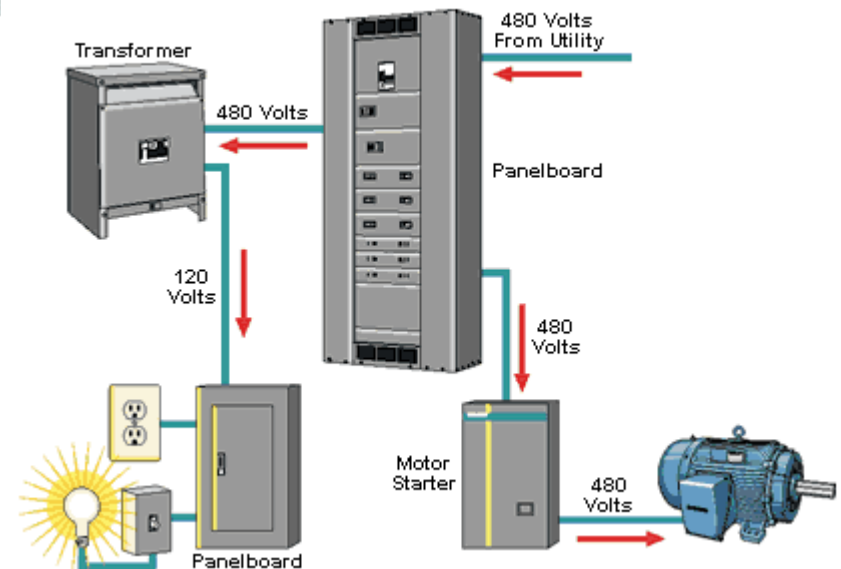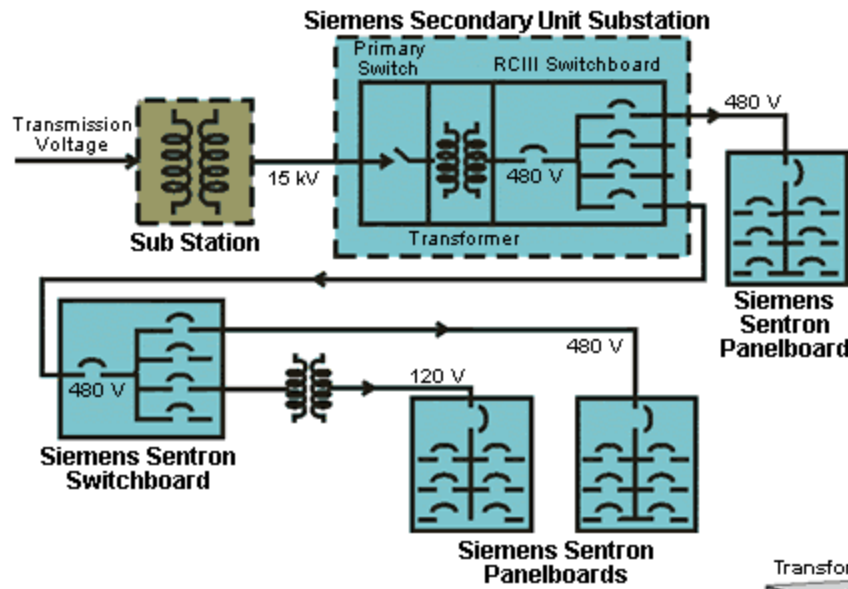


Transformers and 3-phase power

- Three phase wiring

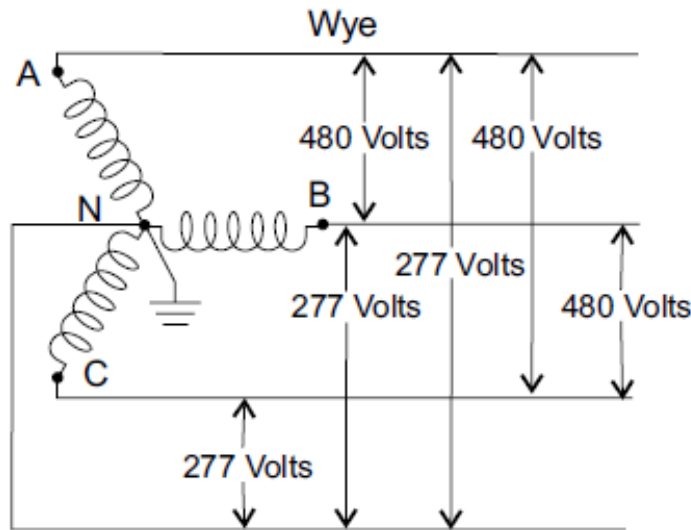

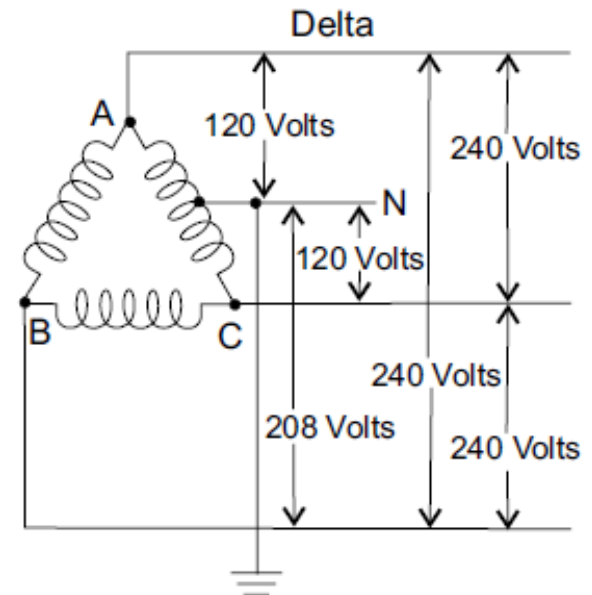A - B 480 Volts
B - C 480 Volts
C - A 480 Volts
A - N 277 Volts
B - N 277 Volts
C - N 277 Volts




A - B 240 Volts
B - C 240 Volts
C - A 240 Volts
A - N 120 Volts
B - N 208 Volts
C - N 120 Volts


Transformers and 3-phase power

- Three phase wiring


480 Delta: 277 WYE

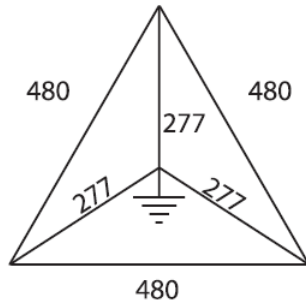


208 Delta: 120 WYE *

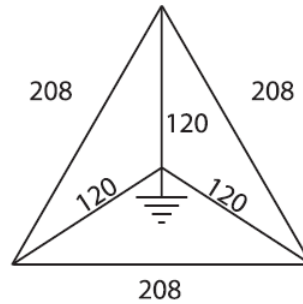


240: 120 Split Phase

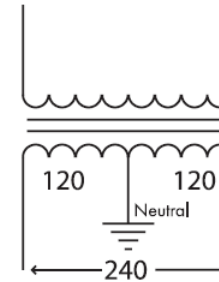


240 Delta: 120 Stinger

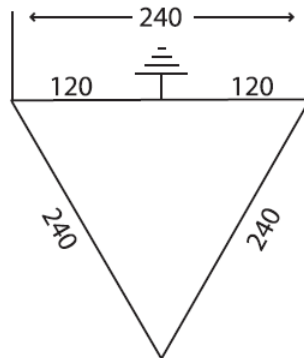

240 Delta


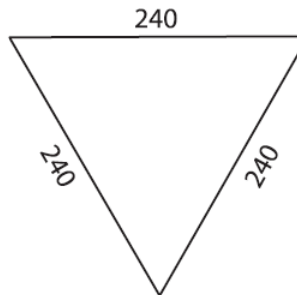


208 Delta *

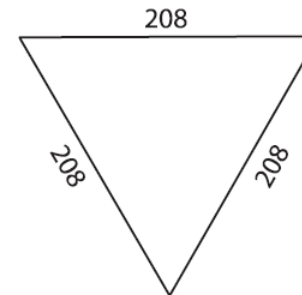


Transformers and 3-phase power

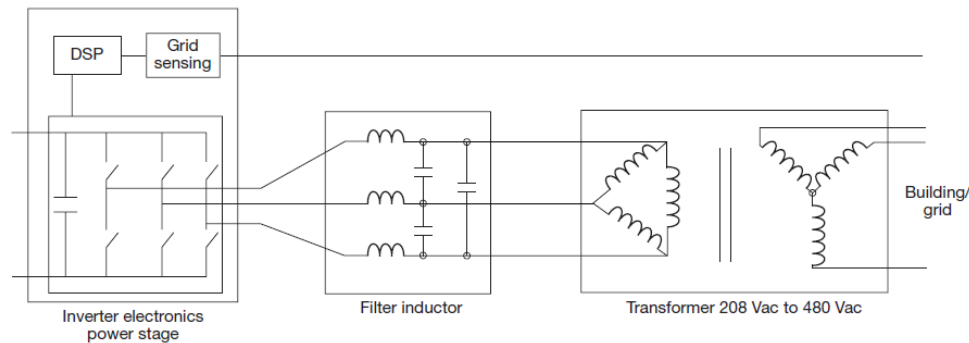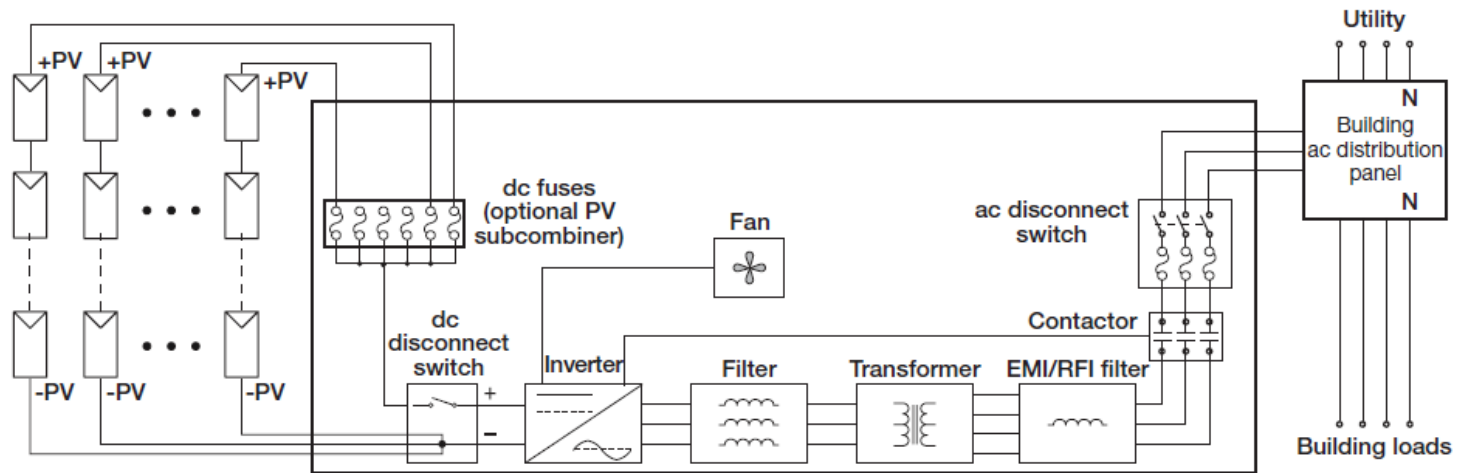- How do we design a 3-phase PV system
- Use a 3-phase inverter



Transformers and 3-phase power

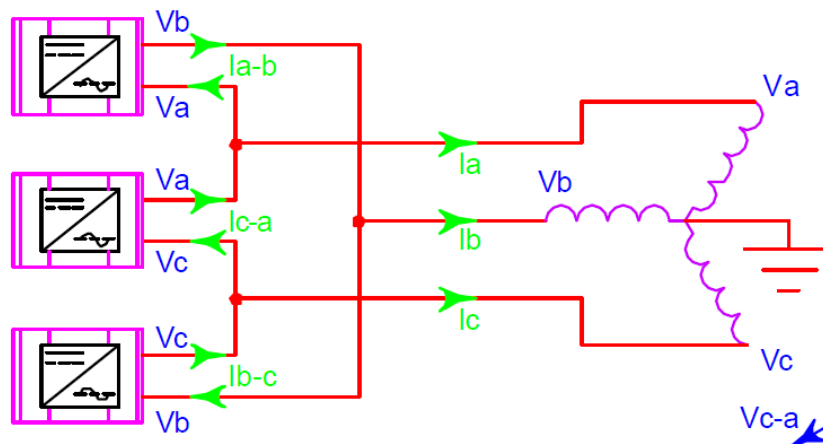- How do we design a 3-phase PV system
- Use multiple single phase inverters



- What is the OCPD rating for inverter output?
(max AC output of SB6000US at 208V = 29A)
 $29A * 1.25 = 36.25A$ next size = 40A
- What is the OCPD rating of each phase? 40A
- What is the OCPD for the 3 phase subpanel?
 $29A * \sqrt{3} = 50.2A * 1.25 = 62.8A$ next size = 70A