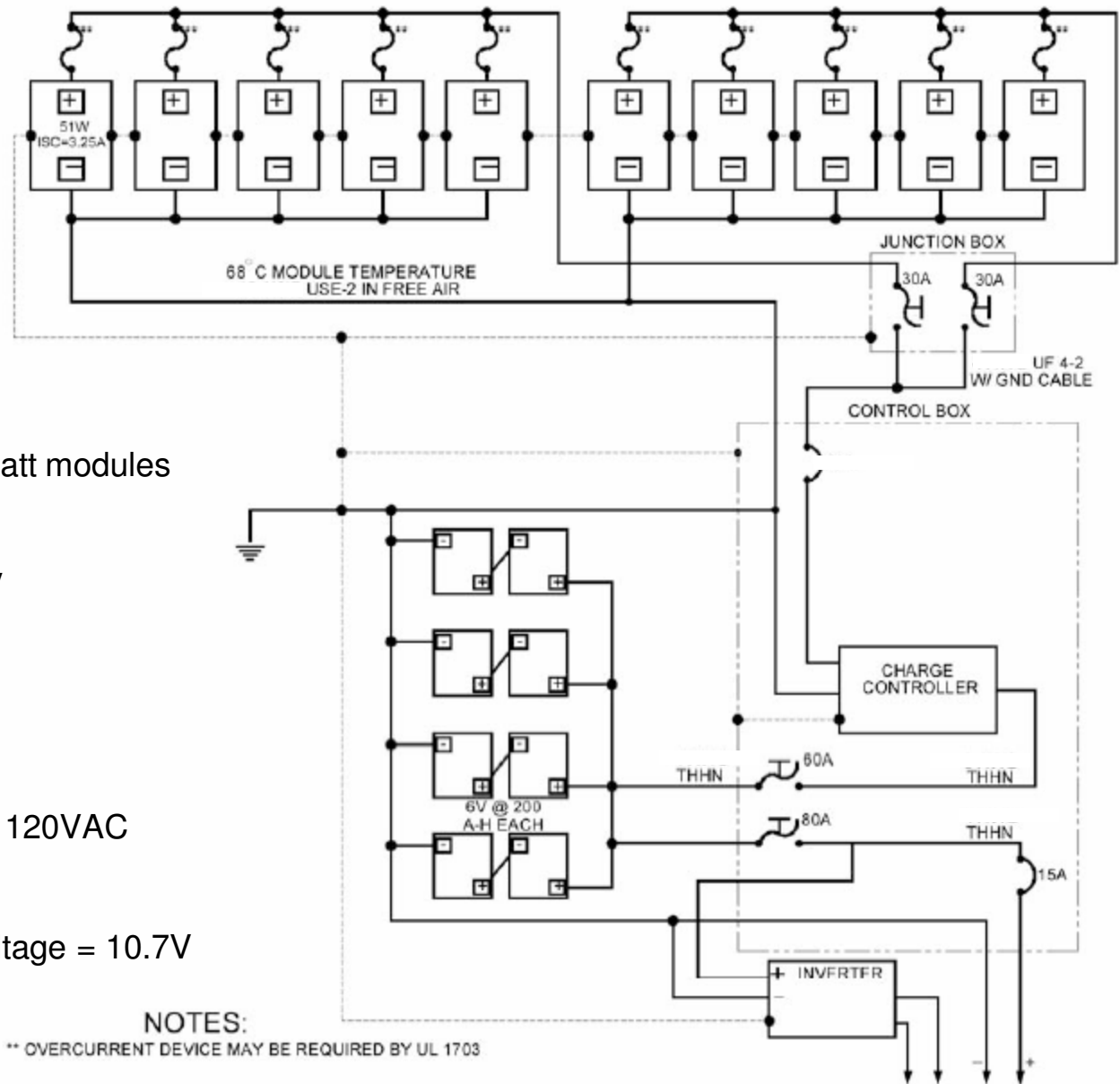


# Cable sizing and over current protection



## Array size:

10 12V, 51Watt modules

ISC = 3.25A

VOC = 20.7V

## Batteries:

800 Ahr, 12V

## Inverter:

500W rating, 120VAC

90% eff

Min input voltage = 10.7V

## NOTES:

\*\* OVERCURRENT DEVICE MAY BE REQUIRED BY UL 1703

# Cable sizing and over current protection

Example 3 (do this as a homework problem):

- Size source circuit conductors for the two sub-arrays  
(USE-2 rated in free air, 68C ambient)
- Size the combined circuit conductors from junction box  
(UF conductor directly buried, 40C ambient)
- Size the inverter output conductor  
(THWN in conduit with 4 current carrying conductors, 40C ambient)
- Size the battery to inverter to conductors  
(THHN in free air, 40C ambient temperature)